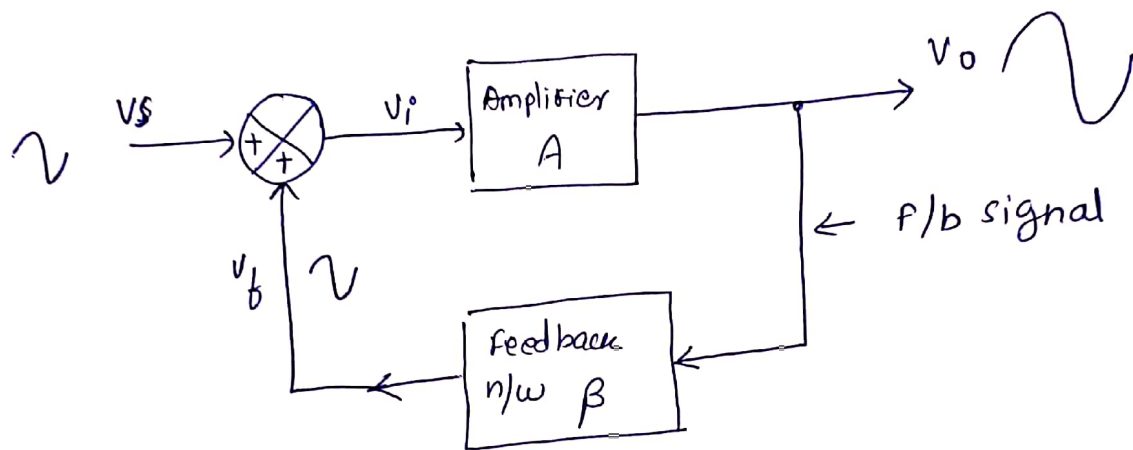


Oscillators

If something is oscillating at a constant frequency, we can generate an oscillator.

Oscillations are everywhere: any signal generated by our body is an oscillation e.g. Brainwaves, ^{ecg}ecg...

Oscillator definition: An oscillator is an amplifier, which uses a positive feedback, and without an external signal, generates an output waveform at a desired frequency.



Consider a non-inverting Δ er with voltage gain A , as shown in the above figure. There is a feedback n/w with feedback factor β . The feedback is said to be positive whenever the part of the output that is fed back into the input is in phase with the original signal applied to the Δ er.

(Note: if the f/b signal is out of phase with ~~the~~ i/p then it will be $V_s - V_f$, only if the f/b signal is in phase with i/p then it will be $V_s + V_f$).

$$V_i = V_s + V_f$$

$$\therefore V_s = V_i - V_f$$

$$= V_i - \beta V_o$$

$$\text{Circuit gain } A_f = \frac{V_o}{V_i - \beta V_o}$$

$$= \frac{V_o/V_i}{1 - \beta(V_o/V_i)}$$


$$= \frac{A}{1 - A\beta}$$

A	β	A_f
20	0.005	22.22
20	0.04	100
20	0.045	200
20	0.05	∞

substitute these values
in the equation

The table shows that the gain with feedback increased as the amount of +ve F/B increased. In the limiting case, the gain becomes infinite. This indicates that circuit can produce output without external input ($V_s = 0$), just by feeding the part of the output as its own input. Similarly, the output cannot be infinite but gets driven into oscillations. In other words, the circuit stops amplifying & starts oscillating.

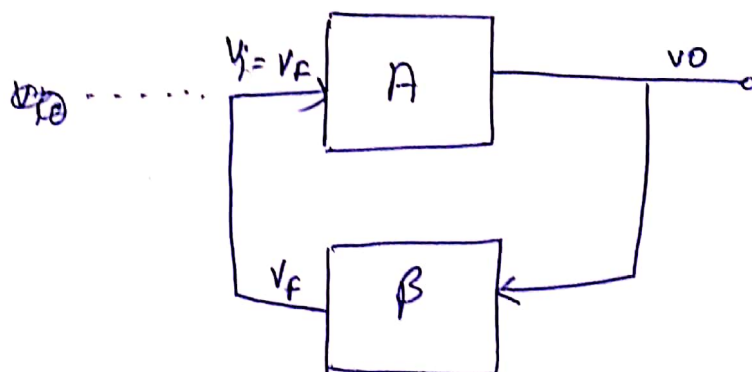Barkhausen criteria for sustained oscillations:



①

$$V_o = A V_i$$

$$V_f = \beta V_o$$

$$\therefore V_f = \beta A V_i$$


$$\text{But } V_i = V_f$$

$$\therefore |A\beta| = 1 \quad \text{--- loop gain}$$


② The phase of V_f should be same as V_i i.e. the f/b n/w should introduce 0° phase shift if the amplifier is non-inverting & 180° phase shift if the amp is inverting to ensure positive feedback.

In practice, $A\beta$ is made greater than 1 to start the oscillations and then the circuit adjusts itself to get $A\beta = 1$, finally resulting into self-sustained oscillations.

$$|A\beta| > 1$$

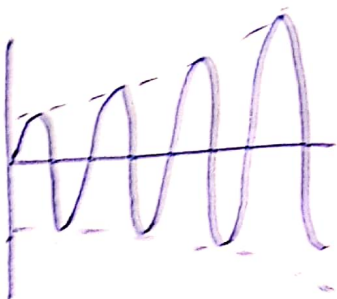

$$|A\beta| = 1$$

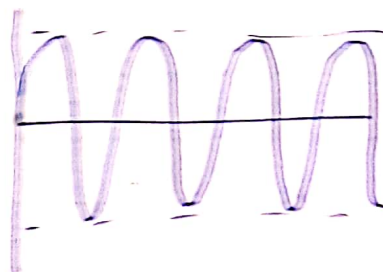

$$|A\beta| < 1$$

