

SVKM's NMIMS
MUKESH PATEL SCHOOL OF TECHNOLOGY MANAGEMENT & ENGINEERING

Programme: MBA Tech (All Streams)

Year: I

Semester: II

Academic Year: 2017-2018

Subject: Basic Electronics

Date: 08 May 2018

Marks: 70

Time: 10.00 am to 1.00 pm

Durations: 3 (hrs)

No. of Pages : 02

Final Examination


Instructions: Candidates should read carefully the instructions printed on the question paper and on the cover of the Answer Book, which is provided for their use.

- 1) Question No. 1 is compulsory.
- 2) Out of remaining questions, attempt any 4 questions.
- 3) In all 5 questions to be attempted.
- 4) All questions carry equal marks.
- 5) Answer to each new question to be started on a fresh page.
- 6) Figures in brackets on the right hand side indicate full marks.
- 7) Assume suitable data if necessary.

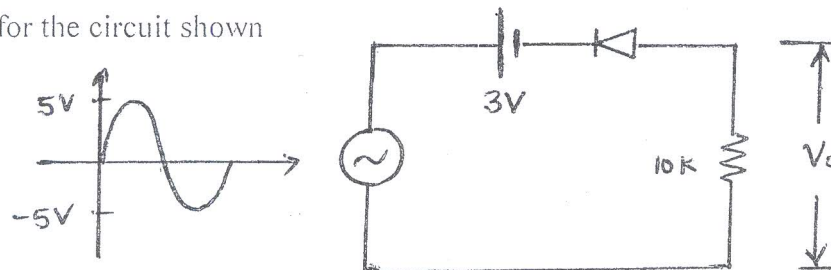Q1. Attempt any four

14

- a Define the common base and common emitter current gain and find the relation between them.
- b Determine V_o for the circuit shown



- c Draw the construction for n-channel D-MOSFET and also draw its transfer characteristics.
- d Explain Barkhausen's criterion for sustained oscillation.
- e Classify the power amplifier based on output waveforms.


Q2a In the voltage regulator circuit shown in figure below $V_i = 20V$, $V_z = 10V$, $R_i = 222\Omega$, 6

$P_{z(max)} = 400 \text{ mW}$,


Determine

i) I_L , I_z , and I_i if $R_L = 380\Omega$,

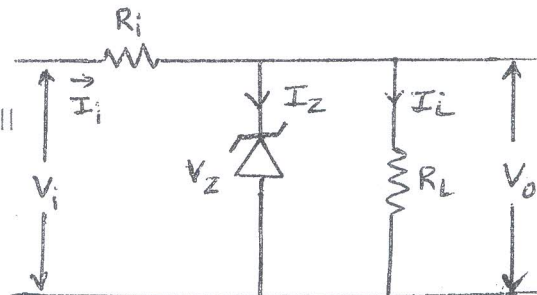
ii) determine the value of R_L that will establish $P_{z(max)}$ in the diode



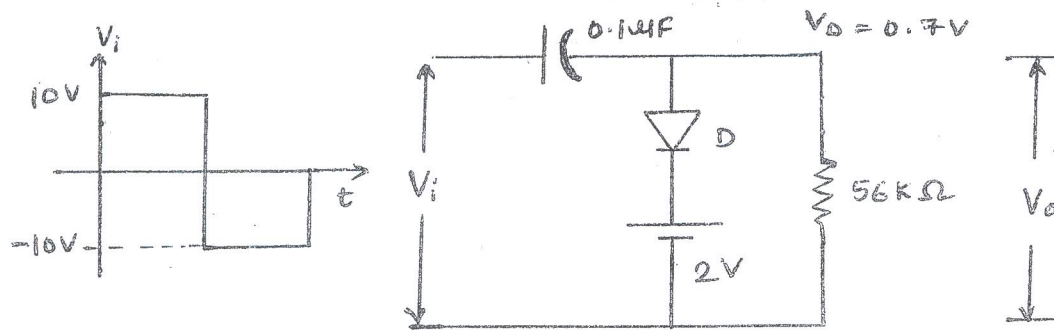- Q2b Explain the operation of C- filter with full wave rectifier 4
- Q2c Determine the output waveform for the circuit shown below 4



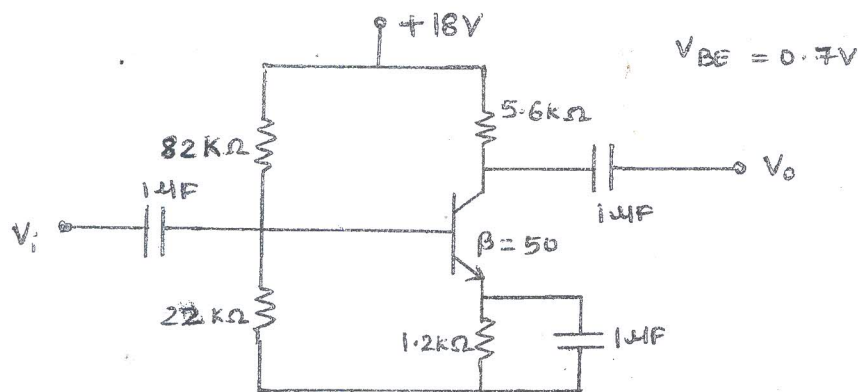
- Q3a Derive the expression for stability factor S_{ICQ} for voltage divider bias. 7
- Q3b Find Q point for the circuit shown. 7



- Q4a Determine Q-point for the circuit shown, 7

$$I_{DSS} = 8\text{mA}$$

$$V_{R_{S(off)}} = -4\text{V}$$

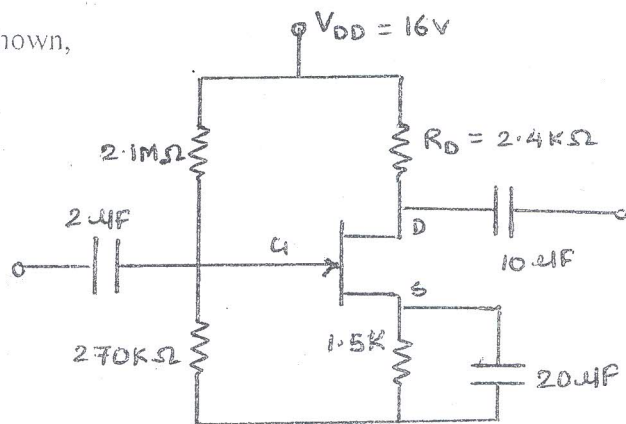

- Q4b Draw and explain the circuit diagram for class A direct coupled power amplifier and write down the expression for its efficiency. 7

- Q5a Draw the circuit-diagram and explain the operation of RC- phase shift oscillator 7

- Q5b Draw the circuit diagram for Hartley's Oscillator and write expression for the frequency of oscillation. 7

- Q6a Compare different rectifier circuits. 7

- Q6b Explain with diagram the class B push pull amplifier and write down the maximum efficiency. 7

- Q7 Write short note on

- a Early effect in BJT 4
- b Schottky diode 5
- c Photo diode 5