

SVKM's NMIMS
MUKESH PATEL SCHOOL OF TECHNOLOGY MANAGEMENT & ENGINEERING

Programme: MBA. Tech (All Streams)

Year: I

Semester: I

Academic Year: 2015-2016

Subject: Basic Electrical Engineering

Date: 30/11/2015

Marks

: 70

Time

: 10.00 am to 1.00 pm

Durations

: 3 (hrs)



Final-Examination

Instruction: Candidates should read carefully the instructions printed on the question paper and on the cover of the Answer Book, which is provided for their use.


NB:

- 1) Question No.1 is compulsory.
- 2) Out of remaining questions, attempt any 4 questions.
- 3) In all 5 questions to be attempted.
- 4) All questions carry equal marks.
- 5) Answer to each new question to be started on a fresh page.
- 6) Figures in brackets on the right hand side indicate full marks.
- 7) Assume Suitable data if necessary

Q.1.


- a) Calculate equivalent resistance between terminals A and B.

[5]

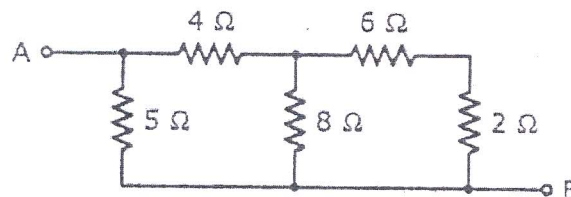

- b) Find voltage V_{AB} using superposition theorem.


[5]

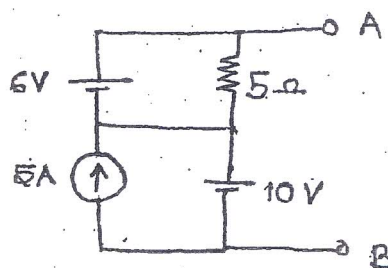

- c) Compare Electrical and Magnetic circuit.


[4]

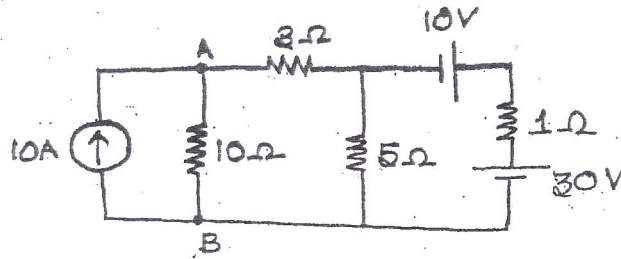Q.2. a) Using source transformation finds the current flowing through the $10\ \Omega$ resistance




b) Find the current flowing through $6\ \Omega$ resistance by using thevenin's theorem.

[7]

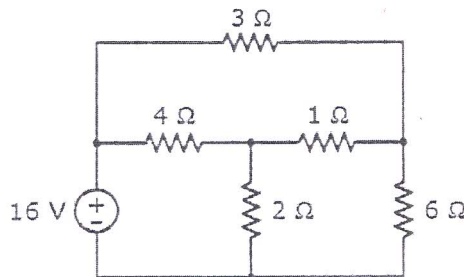

Q.3. a) Find average value of waveform shown.

[2]

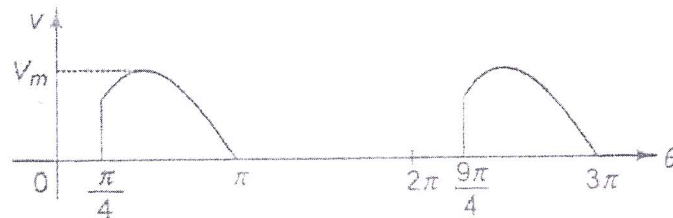


Q.3.b) Why current leads voltage in RC series circuit. Draw phasor diagram and waveforms for voltage and current. [6]

Q.3. c) Explain RLC parallel resonance with the help of circuit diagram, phasor diagram. Find the expression for resonance frequency and dynamic impedance. [6]

Q.4. a) A balanced, three phase load connected in delta draws a power of 10.44 kW at 200 V at a power factor of 0.5 lead. Find the values of the circuit elements and the reactive volt-amperes. [7]

Q.4. b) Find the current through $4\ \Omega$ resistance using Nodal analysis.

[7]

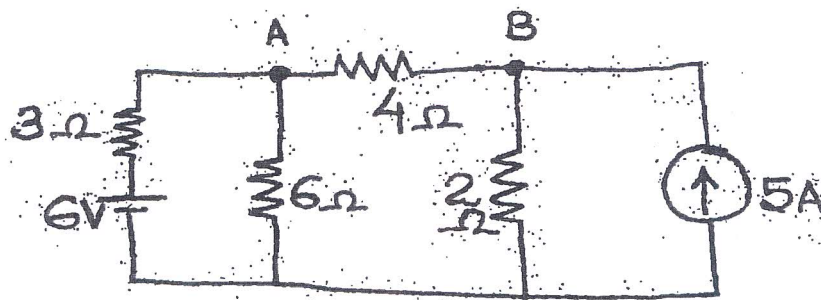

[7]

Q.5 a) An iron ring of mean diameter 22 cm and cross section of 10 cm^2 has an air gap 1 mm wide. The ring is wound uniformly with 200 turns of wire. The permeability of iron is 1000. A flux of 0.16 mWb is required in air gap. What current should be passed through the wire.

Two coils, A of 12500 turns and B of 16,000 turns, lie in parallel planes so that 60 % of flux produced in coil A links coil B. it is found that a current of 5A in A produces a flux of 0.6 mWb while the same current in B produces 0.8 mWb. Determine (i) mutual inductance and coupling coefficient.

Q.6 a) With the help of a neat diagram explain how short circuit test is conducted on a single phase transformer.

[7]

Q.6 b) A 5kVA, 240/2400 V, 50 Hz single phase transformer has the maximum value of flux density as 1.2 Tesla. If the emf per turn is 8 V. calculate number of primary and secondary turns and the primary and secondary current at full load.

[7]

Q.7 a) Derive the emf equation of DC motor.

[4]

Q.7 b) With neat circuit diagram explain the types of DC motor.

[5]

Q.7 c) Explain the working principle and construction of three phase induction motor

[5]