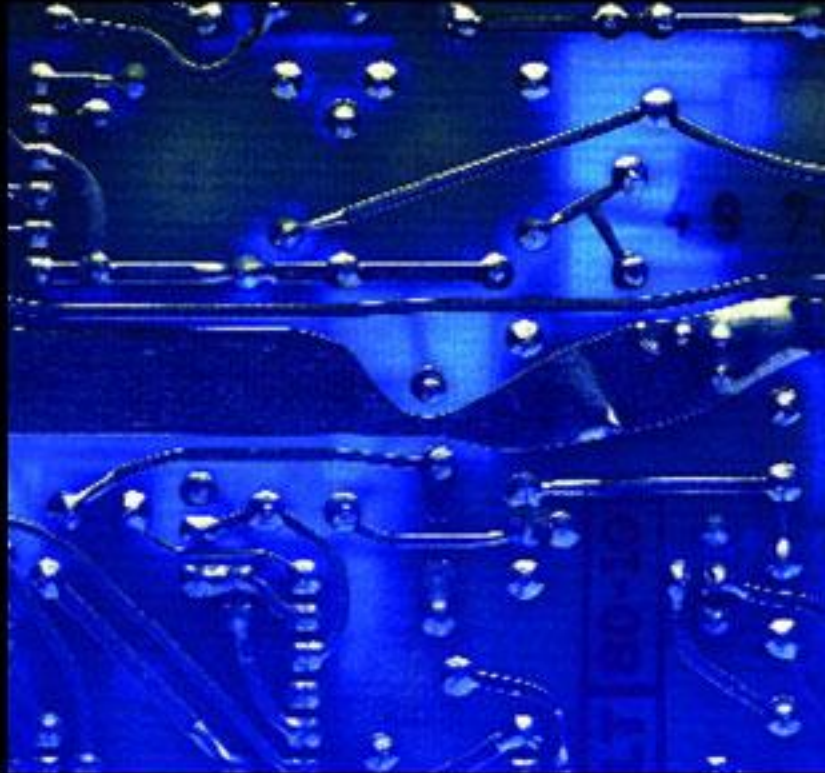


# ELECTRONIC DEVICES AND CIRCUIT THEORY

TENTH EDITION



**BOYLESTAD**

PEARSON

## Chapter 3: Bipolar Junction Transistors

Islamic University of Gaza

**Dr. Talal Skaik**


# Transistor Construction

There are two types of transistors:

- *npn*
- *pnp*


The terminals are labeled:

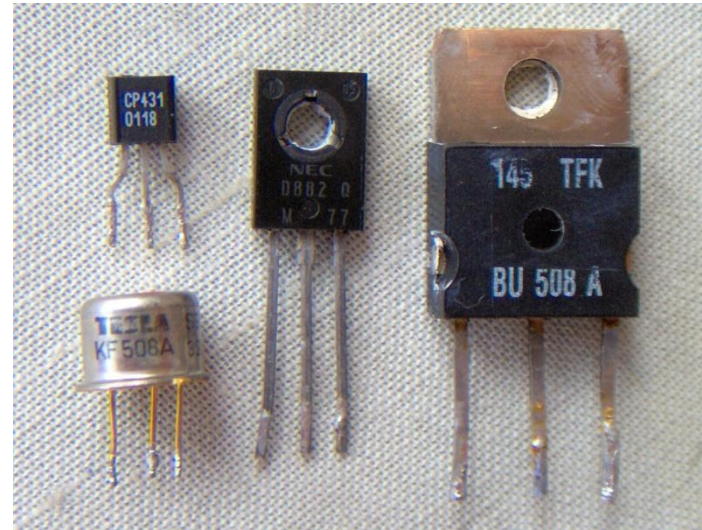- **E - Emitter**
- **B - Base**
- **C - Collector**




- The *npn* BJT consists of three semiconductor regions: the emitter region (*n type*), the base region (*p type*), and the collector region (*n type*).
- The *pnp* BJT consists of three semiconductor regions: the emitter region (*p type*), the base region (*n type*), and the collector region (*p type*).


# Transistor Construction

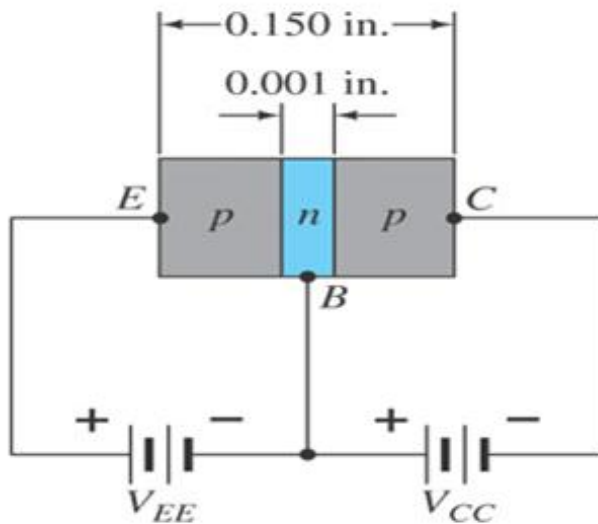


**pnp**

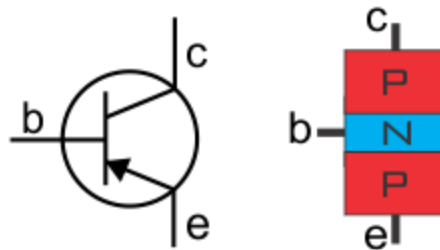

PNP TRANSISTOR

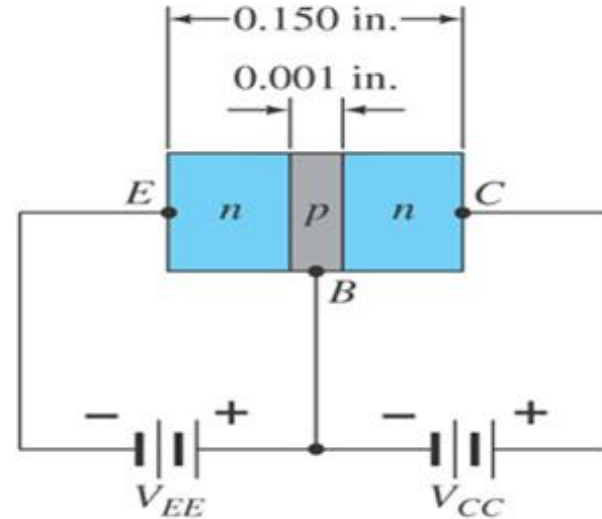

**npn**

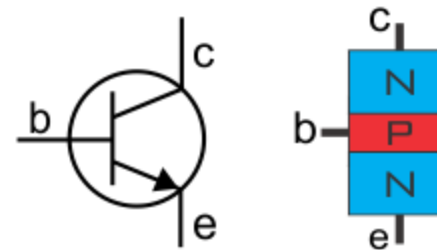

NPN TRANSISTOR

The transistor consists of two *pn junctions*, the **emitter–base junction (EBJ)** and the **collector–base junction (CBJ)**.

# Transistor Construction

- **Emitter**: The portion on one side of transistor that supplies charge carriers (i.e. electrons or holes) to the other two portions.
- The emitter is a heavily doped region.
- Emitter of PNP transistor supplies hole charges to its junction with the base. Similarly, the emitter of NPN transistor supplies free electrons to its junction with the base.

# Transistor Construction

- ❑ **Collector** is the portion on the other side of the transistor (i.e. the side opposite to the emitter) that collects the charge carriers (i.e. electrons or holes).
- ❑ The doping level of the collector is in between the heavily doping of emitter and the light doping of the base.
- ❑ **Base:** The middle portion which forms two PN junctions between the emitter and the collector is called the base.
- ❑ The base of transistor is thin, as compared to the emitter and is a lightly doped portion.
- ❑ The function of base is to control the flow of charge carrier.

# BJT Modes Of Operation

- There are two junctions in bipolar junction transistor.
- Each junction can be forward or reverse biased independently.
- Thus there are different modes of operations:

**Forward Active.**

**Cut off.**

**Saturation.**

Mode	EBJ	CBJ
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Saturation	Forward	Forward

# BJT Modes Of Operation

## FORWARD ACTIVE

- Emitter-base junction is forward biased and collector-base junction is reverse biased.
- The BJT can be used as an amplifier and in analog circuits.

## CUTT OFF


- When both junctions are reverse biased it is called cut off mode.
- In this situation there is nearly zero current and transistor behaves as an open switch.

## SATURATION


- In saturation mode both junctions are forward biased.
- Large collector current flows with a small voltage across collector base junction.
- Transistor behaves as an closed switch.


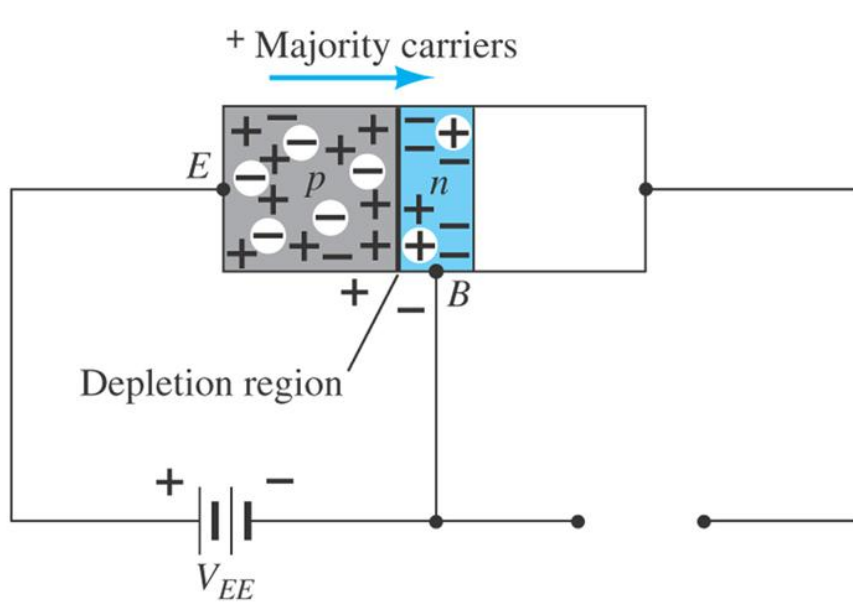
# Operation of pnp transistor in active mode



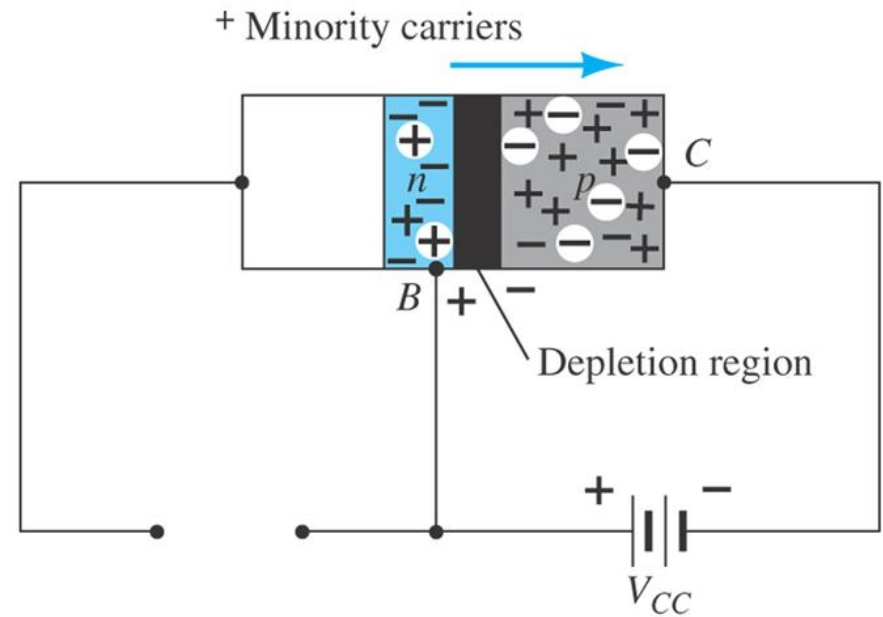**Forward-biased junction of a pnp transistor.**




**Reverse-biased junction of a pnp transistor**


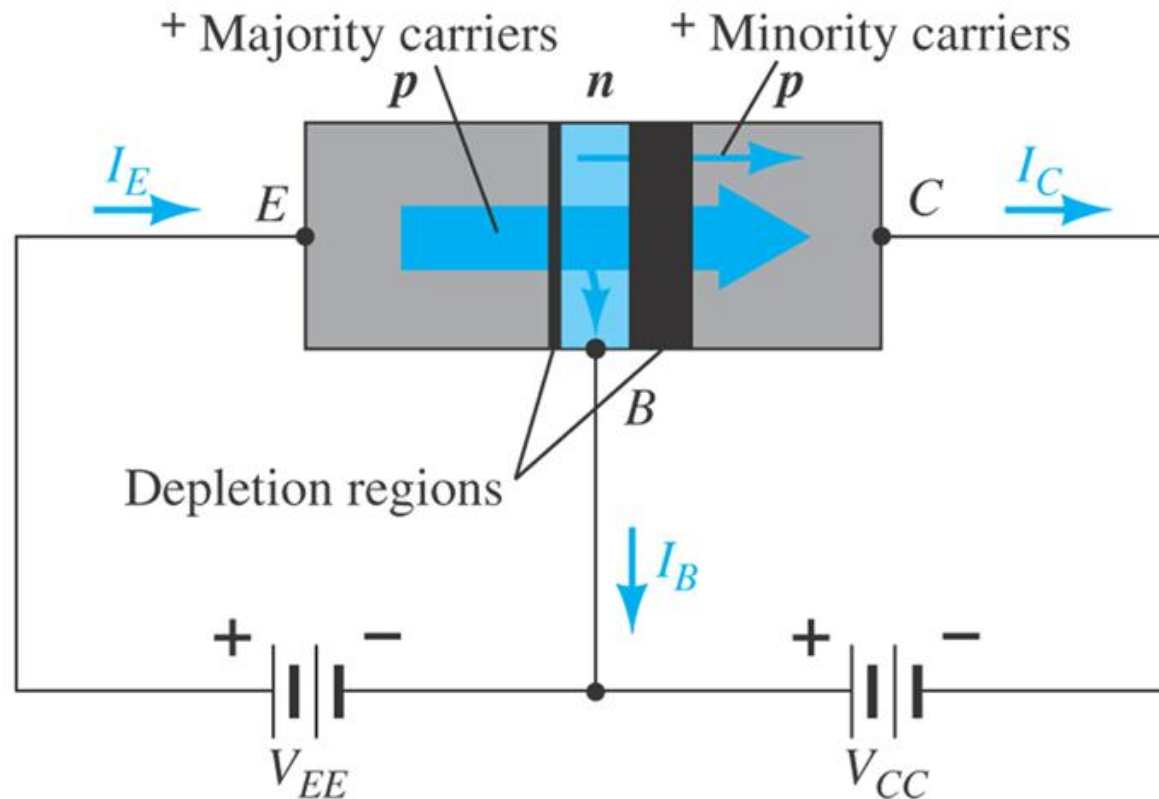
# Operation of pnp transistor in active mode

With the external sources,  $V_{EE}$  and  $V_{CC}$ , connected as shown:


- The emitter-base junction is forward biased
- The base-collector junction is reverse biased



# Currents in a Transistor

Emitter current is the sum of the collector and base currents:

$$I_E = I_C + I_B$$

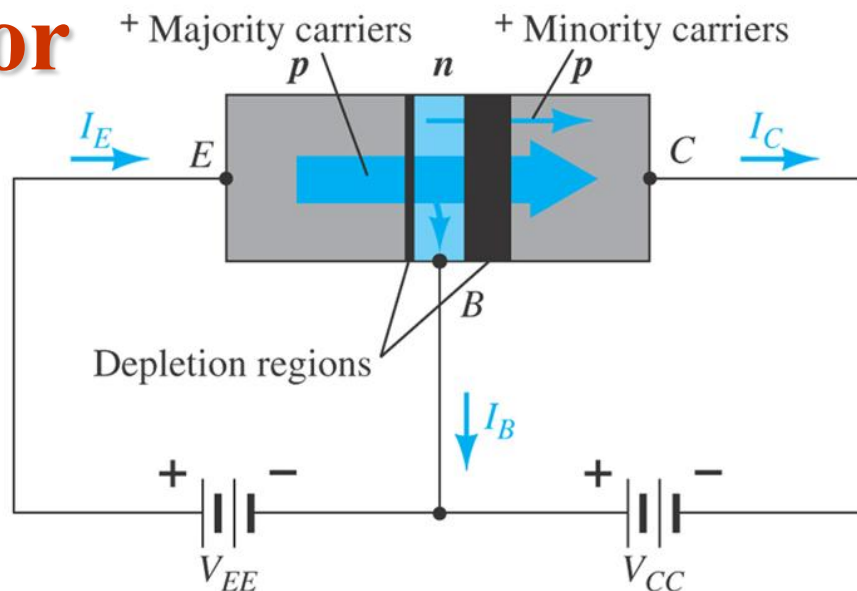


The collector current is comprised of two currents:






$$I_C = I_{C_{\text{majority}}} + I_{C_{\text{minority}}}$$

The minority current is called the leakage current and is given by the symbol  $I_{CO}$  ( $I_C$  current with emitter terminal **O**pen).

# Common Base Configuration

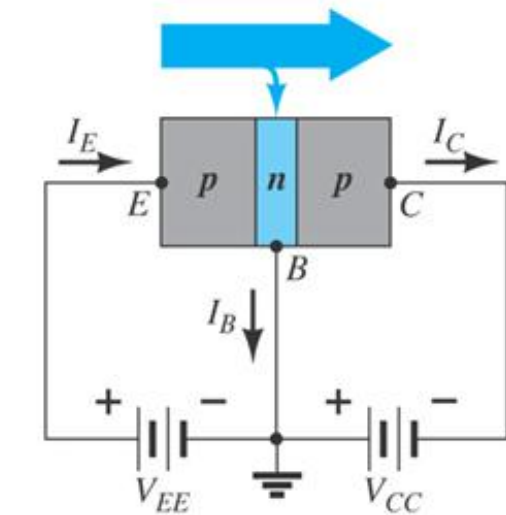

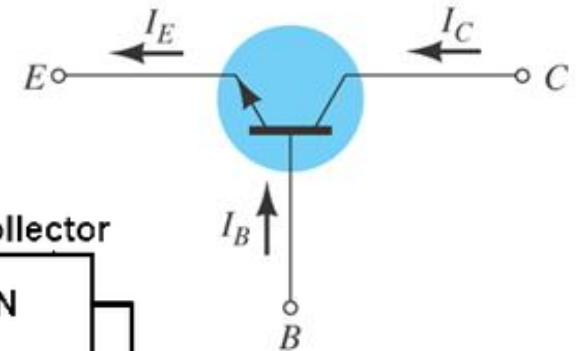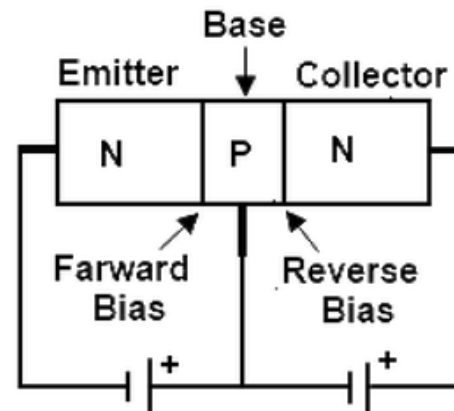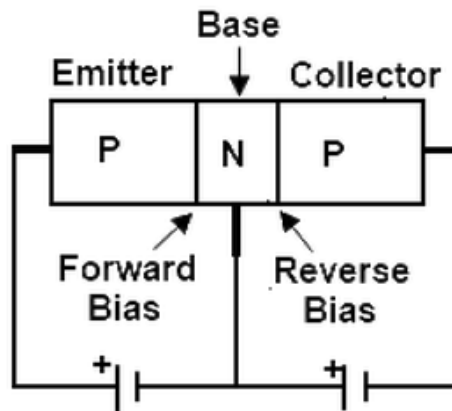
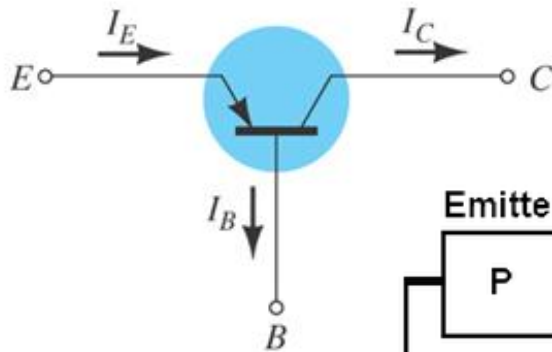
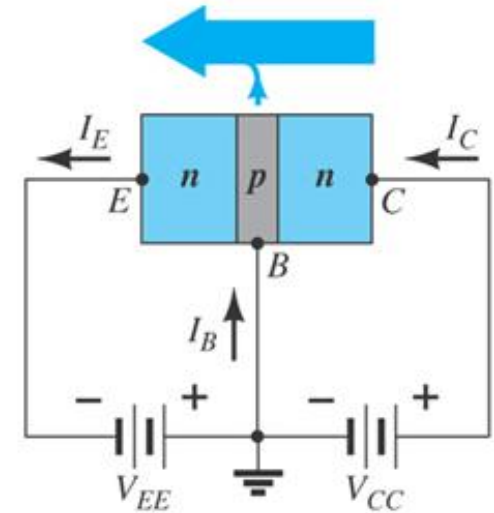
The base is common to both input (emitter–base) and output (collector–base) of the transistor.





# Common-Base Configuration
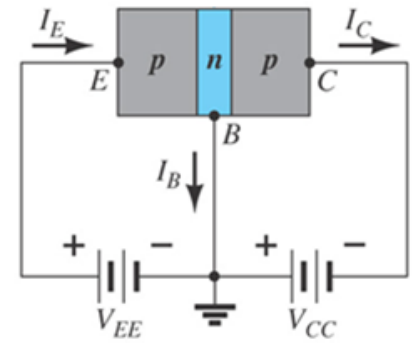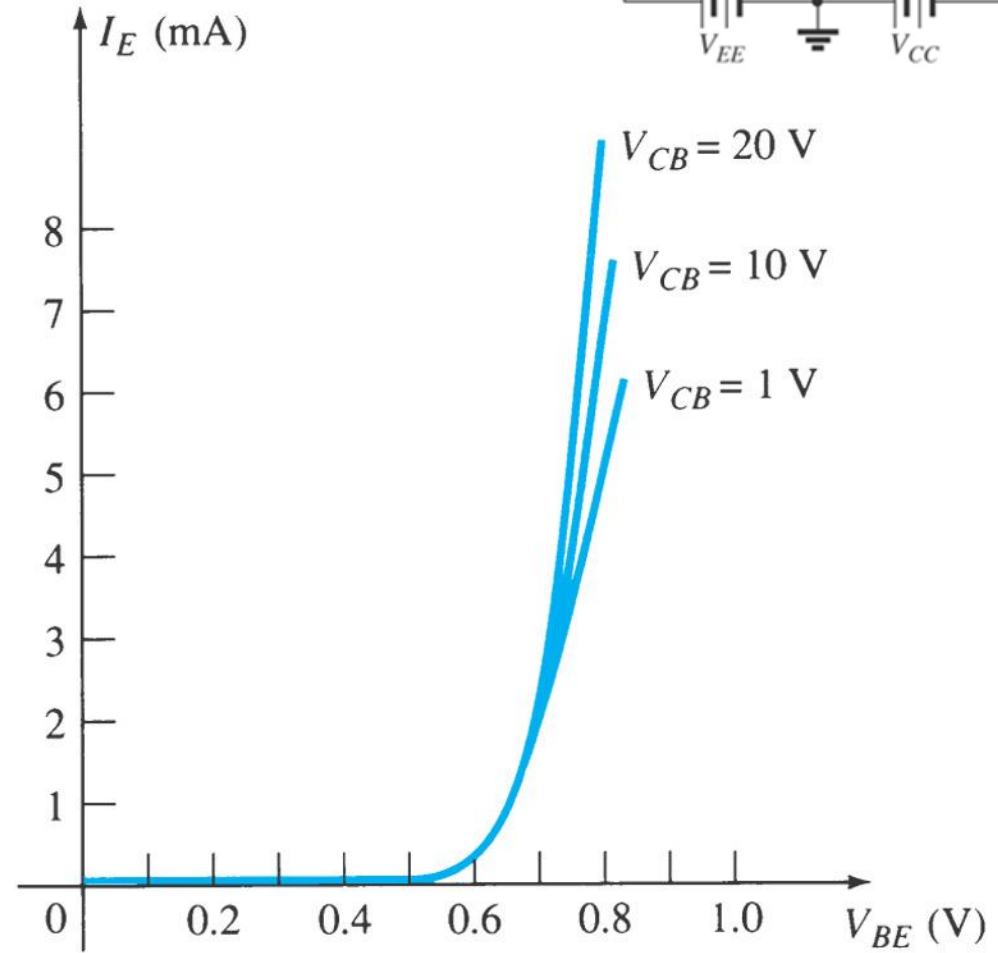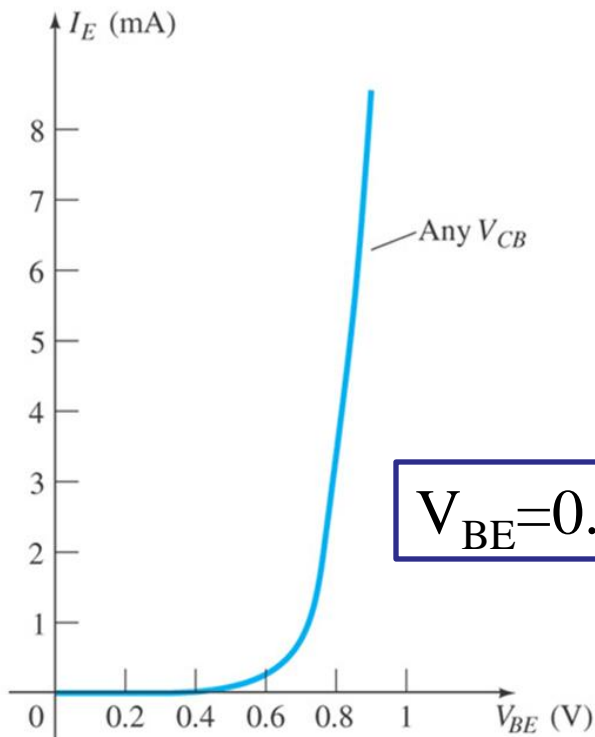
## Input Characteristics

This curve shows the relationship between of input current ( $I_E$ ) to input voltage ( $V_{BE}$ ) for three output voltage ( $V_{CB}$ ) levels.



# Common-Base Configuration

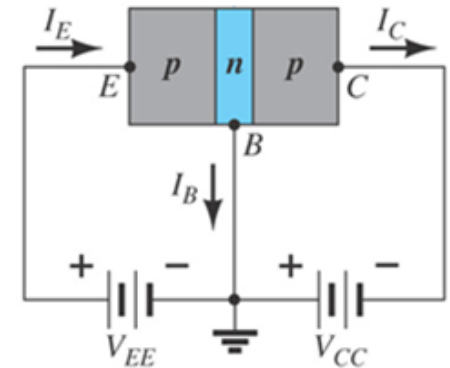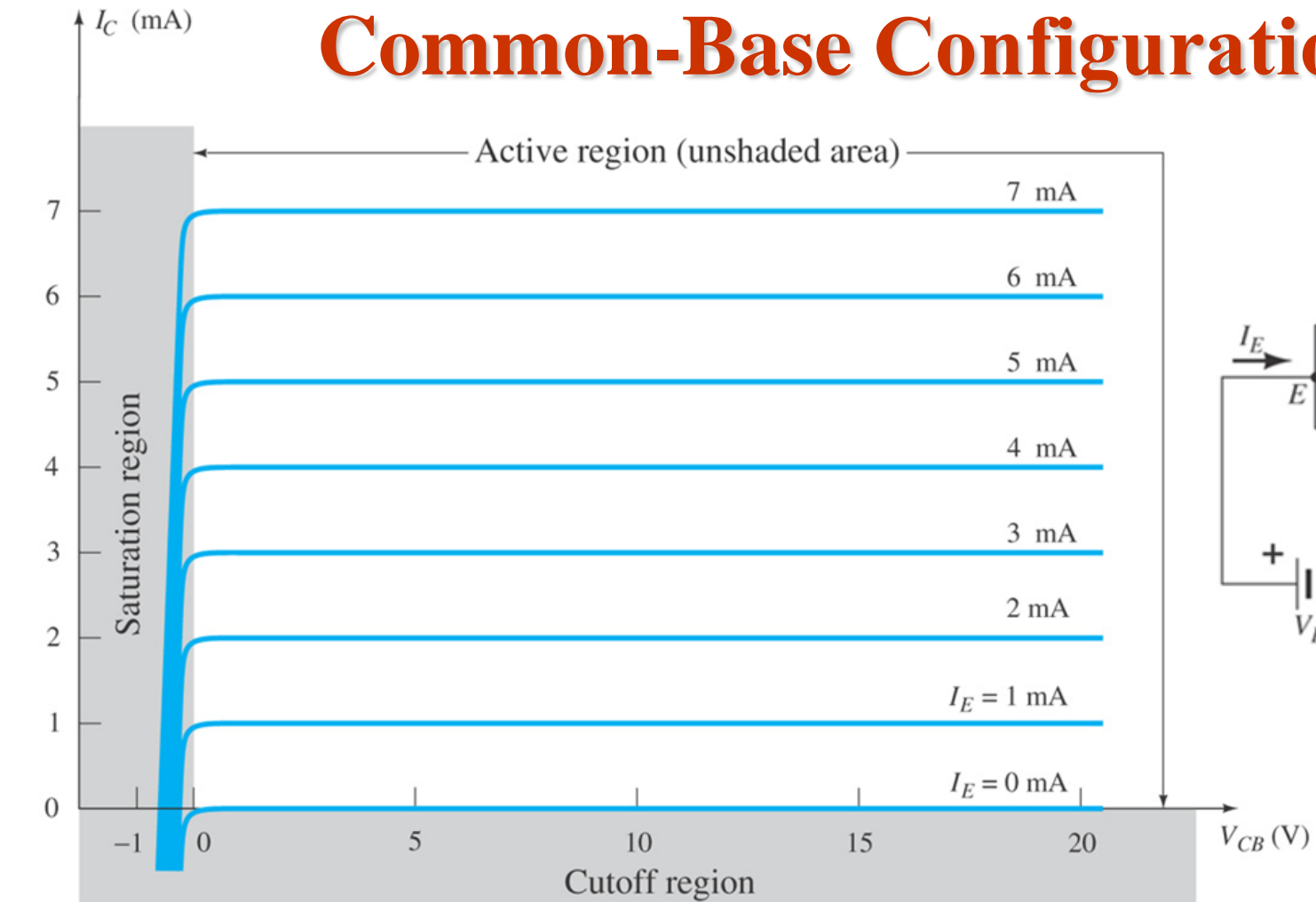


## Output Characteristics

This graph demonstrates the output current ( $I_C$ ) to an output voltage ( $V_{CB}$ ) for various levels of input current ( $I_E$ ).
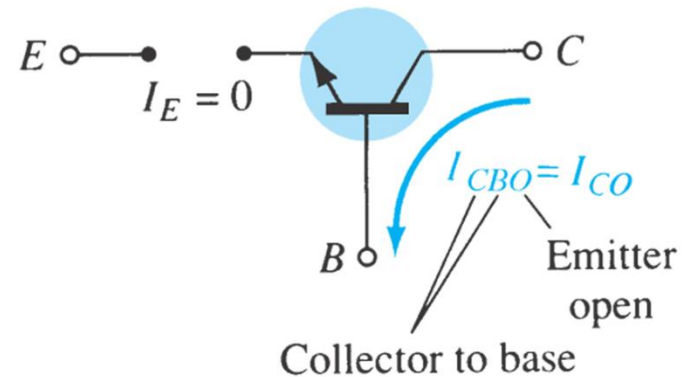
# Operating Regions

- **Active** – Operating range of the amplifier. It is noticed that  $I_E$  is approximately equal to  $I_C$  ( $I_C \approx I_E$ ).
- **Cutoff** – the region where the collector current is approximately 0A ( $I_C = I_{CBO}$ ). The amplifier is basically off. There is voltage, but little current.



- **Saturation** – Region to the left of  $V_{CB} = 0$ . Note the exponential increase in collector current as the voltage  $V_{CB}$  increases toward 0 V. There is current but little voltage.

# Approximations

**Emitter and collector currents:**

$$I_C \cong I_E$$

**Base-emitter voltage:**

$$V_{BE} = 0.7 \text{ V (for Silicon)}$$



# Alpha ( $\alpha$ )

Alpha ( $\alpha$ ) is the ratio of  $I_C$  to  $I_E$ :

$$\alpha_{dc} = \frac{I_C}{I_E}$$

$$I_C = \alpha I_E + I_{CBO}$$

**Ideally:  $\alpha = 1$**

**In reality:  $\alpha$  is between 0.9 and 0.998**

**Alpha ( $\alpha$ ) in the AC mode:**

$$\alpha_{ac} = \left. \frac{\Delta I_C}{\Delta I_E} \right|_{V_{CB} = \text{constant}}$$