

**SVKM's NMIMS**  
**MUKESH PATEL SCHOOL OF TECHNOLOGY MANAGEMENT & ENGINEERING**

Programme: MBA Tech (All Streams)

Year: I

Semester: I

**Academic Year: 2015-16**

Batch: 2014-15


Subject: Basic Electrical Engineering

Date: 10 June 2016

Marks: 60

Time: 10.00 am - 1.00 pm

Duration: 3 Hrs

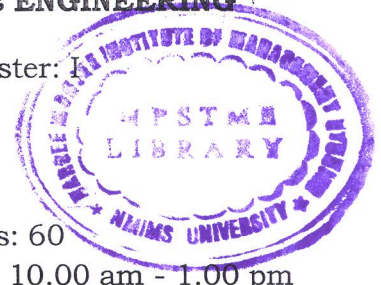

**Re-Examination**


**Instructions:** Candidates should read carefully the instructions printed on the question paper and on the cover of the Answer Books, which is provided for their use.

1. Question No. 1 is compulsory.
2. Out of remaining six questions, attempt any four questions.
3. In all five questions to be attempted
4. Answer to each new questions to be started on a fresh page.
5. Assume suitable data if necessary with proper justifications.


**Q1) Attempt ANY FOUR of the following:**

- |  |    |
|--|----|
| a) State and explain Kirchoff's Laws.                                    | 03 |
| b) Define Frequency, Time Period & Amplitude w.r.t alternating quantity. | 03 |
| c) Compare Electrical and Magnetic circuit.                              | 03 |
| d) Explain in brief working of an ideal transformer.                     | 03 |
| e) With neat diagrams classify different types of DC motors.             | 03 |

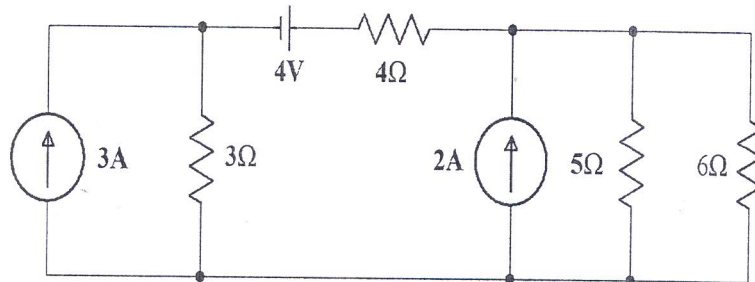
**Q2) a) Analyze the given circuit and evaluate the current flowing through  $6\Omega$  resistor using Thevenin's theorem. 06**



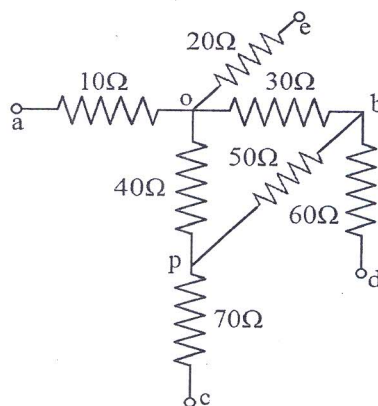**b) Evaluate the equivalent resistance  $R_{AB}$ ,  $R_{AD}$ ,  $R_{AC}$  &  $R_{AE}$  of the given circuit. 06**




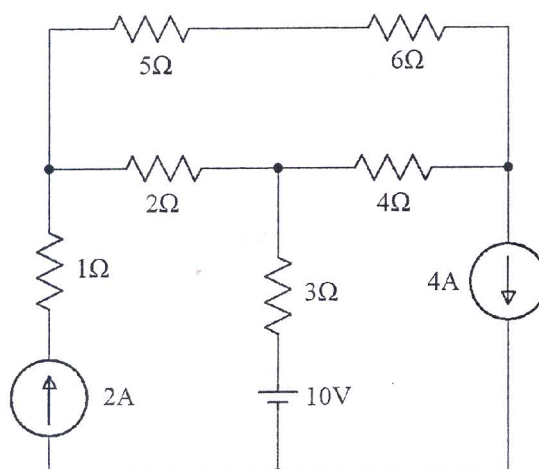- Q3)** a) Analyze the given circuit and evaluate the current flowing through  $6\Omega$  resistor using Superposition theorem. 06



- b) Consider a series RL circuit connected across a AC voltage source, derive the expressions for voltage and current for the circuit also draw phasor diagram with expression for phase difference, impedance and power of the circuit. 06

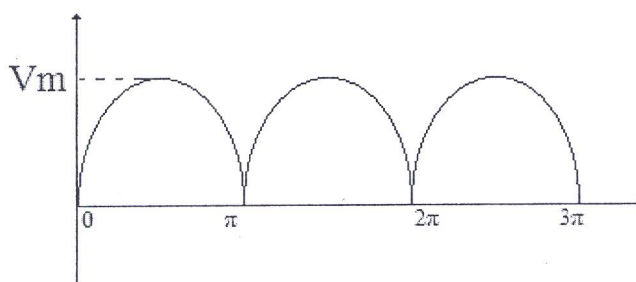- Q4)** a) Find  $V_{avg}$  and  $V_{rms}$  of the given waveform. 06



- b) A R-L-C series circuit with resistance of  $10\Omega$ , inductance of  $0.2H$  and capacitance of  $40\mu F$  is supplied with the  $100V$  supply at variable frequency, Find: 06
- Resonant Frequency
  - Current at resonance
  - Power
  - Power factor
  - Voltage across R, L and C
  - Quality Factor
  - Bandwidth

- Q5)** a) State and explain Faraday's laws of electromagnetic induction also explain self and mutual inductance. 06

- b) Draw phase diagram for transformer at full load considering the losses. (Inductive load) 06

- Q6)** a) Derive relationship between voltage and current for 3- phase star connected supply with balanced inductive load. 06

- b) Explain how rotating magnetic field is setup in 3 phase induction motor. 06

**Q7) Attempt ANY THREE**

- a) State Maximum power transfer theorem, also derive the condition for the same. 04
- b) State and explain all the advantages of three phase supply. 04
- c) Compare Ideal and Practical Transformer. 04
- d) Explain construction and working of a DC Motor. 04

