
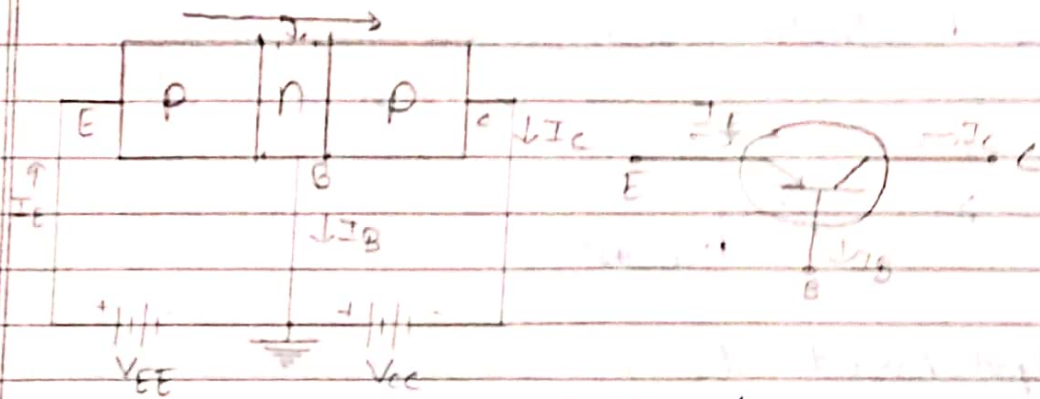



QL

 

PNP Configuration



NPN Configuration

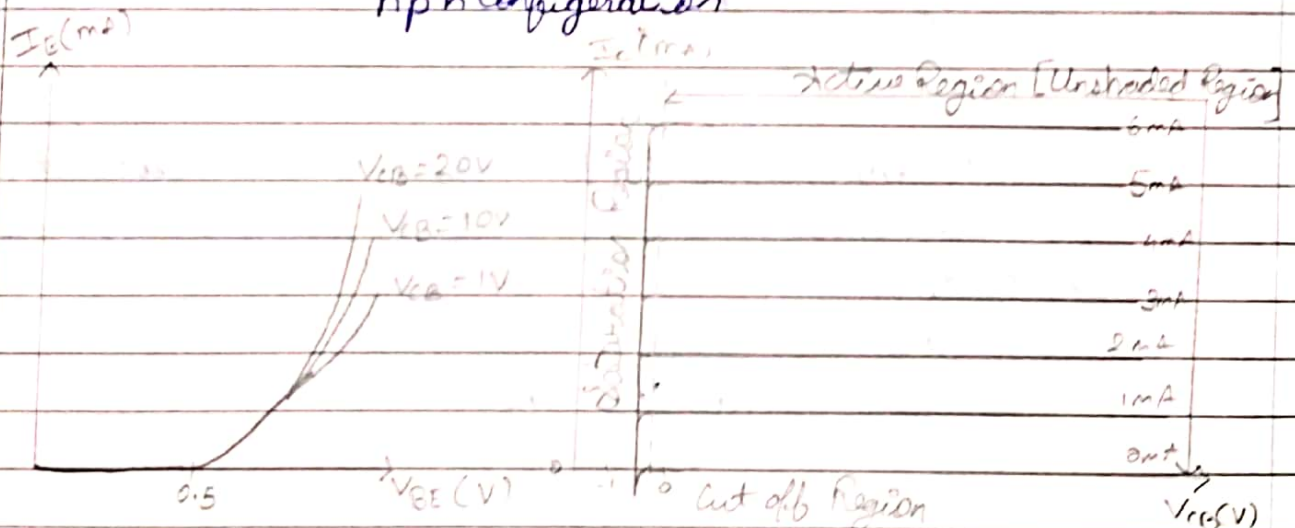

Input Charac.

Output Charac.

Input Characteristic: It is the ratio of change in emitter-base voltage $[\Delta V_{EB}]$ to the resulting change in emitter current $[\Delta I_E]$ at constant collector-base voltage $[V_{CB}]$

$$r_i = \frac{\Delta V_{BE}}{\Delta I_E} \Big|_{V_{CB} = \text{const.}}$$

Output Characteristic: It is the curve between collector base voltage $[V_{CB}]$ and collector current $[I_C]$. From the plot few points can be noted


- Current I_C varies with V_{CB} at only few voltages $[V_{CB} \text{ voltage}]$ and the transistor is never operated in this region
- When the value of V_{CB} is raised above 1-2 V, the collector current becomes ~~almost~~ constant which is indicated as a straight line in graph which means that now I_C is independent on V_{CB} and depends upon I_E only.

$$r_o = \frac{\Delta V_{CB}}{\Delta I_C} \Big|_{I_E = \text{const.}}$$


Current Amplification $[\alpha]$: Change in collector current to the change in emitter current keeping collector base voltage constant.

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \Big|_{V_{CB} = \text{const.}}$$


Q2.

 

npn Configuration

 

pnp Configuration

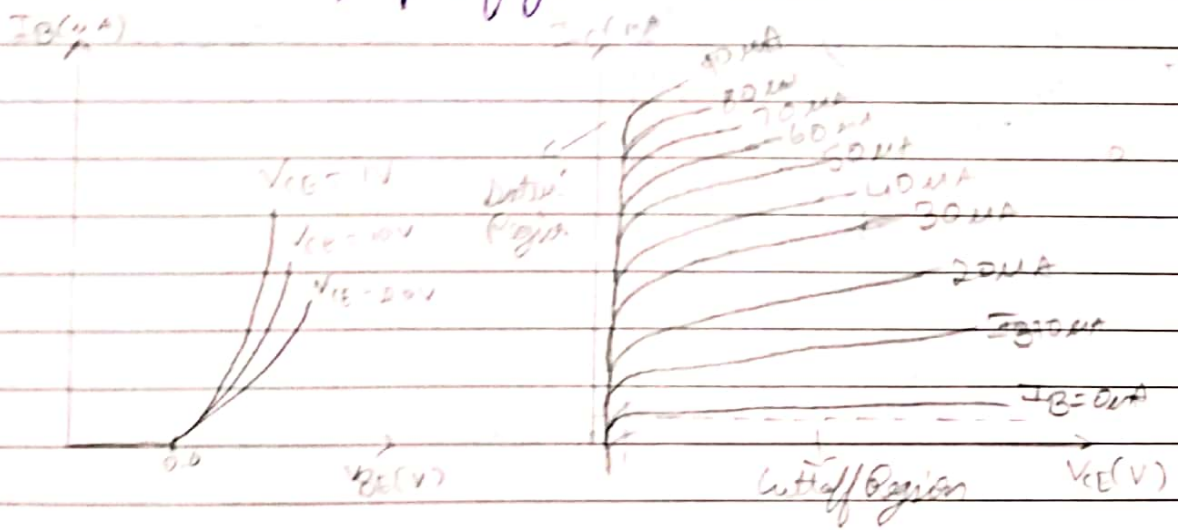

Input Characteristic: Following points can be noted from the graph:-

- The characteristic resembles that of a forward bias diode curve. This is expected since the BE section of transistor is in forward bias.
- I_B increases less rapidly with V_{BE} as compared to CB configuration. Therefore, input characteristic is higher in CE as compared to CB.

$$r_i = \left. \frac{\Delta V_{BE}}{\Delta I_B} \right|_{V_{CE} = \text{const.}}$$

Output Characteristic: The collector current I_C varies with V_{CE} with between 0 to 1 V. After this the collector current almost becomes constant and independent of V_{CE} . This value of V_{CE} upto which collector region I_C changes with V_{CE} is called knee voltage. The transistor is always operated above knee voltage. In this the I_C is almost const.

$$I_C \approx \beta I_B$$


$$\beta = \frac{I_C}{I_B}$$

$$r_o = \left. \frac{\Delta V_{CE}}{\Delta I_C} \right|_{I_B = \text{const.}}$$

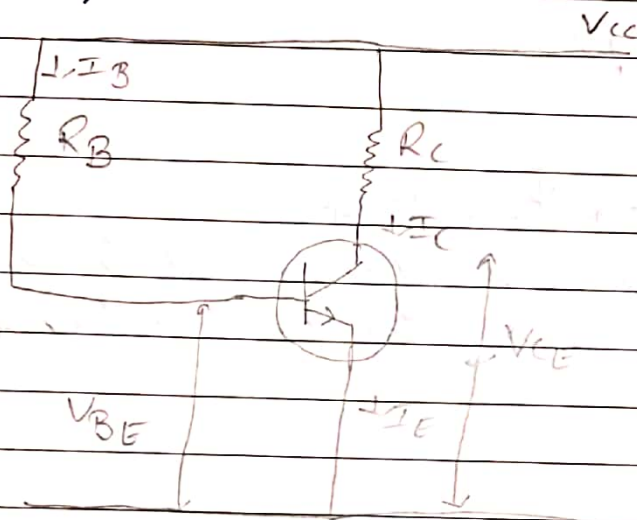Q3.

FIXED BIAS

In this method, a resistor R_B of high resistance is connected in base, as the name implies. The required zero signal base current is provided by V_{CC} which flows through R_B . The base-emitter junction is forward bias, as base is positive with respect to emitter.



Let, I_C be the required signal collector current so,

$$I_B = \frac{I_C}{\beta}$$

Applying KVL

$$V_{CC} = I_B R_B + V_{BE}$$

$$\Rightarrow I_B R_B = V_{BE} \rightarrow V_{CC} - V_{BE}$$

$$\Rightarrow R_B = \frac{V_{CC} - V_{BE}}{I_B}$$

$$\because V_{BE} \ll V_{CC}$$

$$\therefore R_B = \frac{V_{CC}}{I_B}$$

Advantages


- Circuit is simple
- Only one resistor R_E is required
- No Load Effect

Disadvantages

- Stabilisation is poor.

COLLECTOR-BASE BIAS

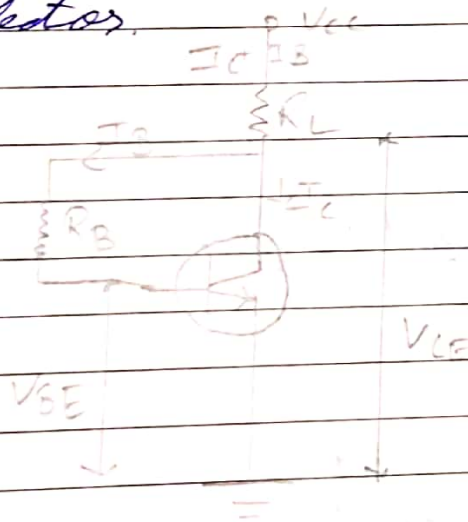The circuit is same as fixed bias but the only difference is the base resistor R_B is returned to the collector.



Voltage drop across R_L

$$R_L = (I_C + I_B)R_L \approx I_C R_L \quad [\because I_B \approx 0]$$

From Figure

$$I_C R_L + I_B R_B + V_{BE} = V_{CC}$$

$$\Rightarrow I_B R_B = V_{CC} - V_{BE} - I_C R_L$$

FOR EDUCATIONAL USE

$$\Rightarrow R_B = \frac{V_{CC} - V_{BE} - I_C R_L}{I_B}$$

Applying KVL


$$(I_B + I_C) R_L + I_B R_B + V_{BE} = V_{CC}$$

$$\Rightarrow I_B (R_L + R_B) + I_C R_L + V_{BE} = V_{CC}$$

$$\therefore I_B = \frac{V_{CC} - V_{BE} - I_C R_L}{R_L + R_B}$$

POTENTIAL DIVIDER BIAS

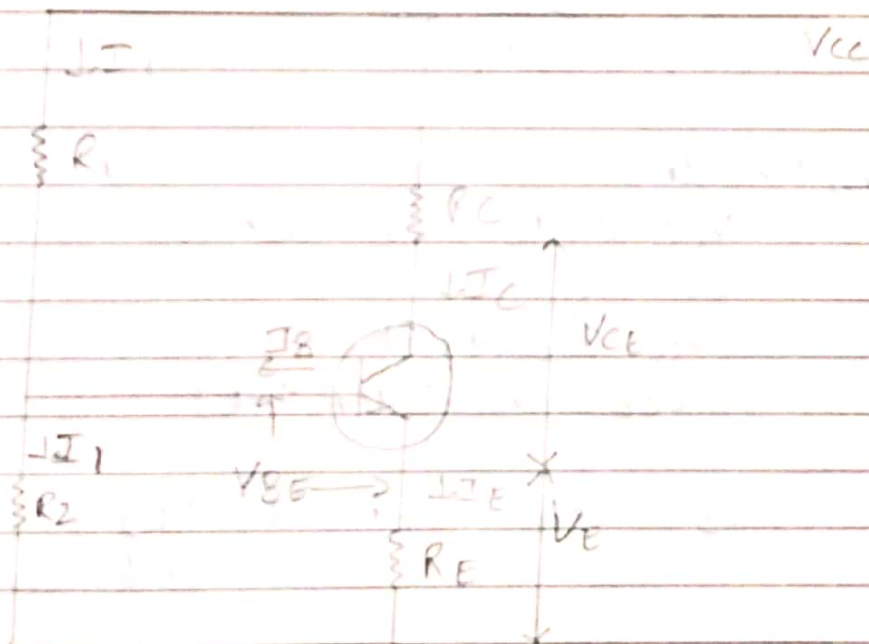Among all of these methods, the potential divider bias is the most prominent one. Here, we use 2 resistors R_1 and R_2 which are connected to V_{CC} and are providing biasing.



$$I_1 = \frac{R V_{CC}}{R_1 + R_2}$$

Voltage across R_2

$$V_2 = \left(\frac{V_{CC}}{R_1 + R_2} \right) R_2$$

Applying KVL to base circuit

$$V_2 = V_{BE} + V_E$$

$$V_2 = V_{BE} + I_E R_E$$

$$I_E = \frac{V_2 - V_{BE}}{R_E}$$

$$\therefore I_E \approx I_C$$

$$\therefore I_C = \frac{V_2 - V_{BE}}{R_E}$$

Applying KVL to collector side

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$


$$\therefore I_C \approx I_E$$

$$\therefore V_{CC} = I_C (R_C + R_E) + V_{CE}$$

$$\therefore V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$V_2 = V_{BE} + I_C R_E \quad [\because R_E \text{ provides best stabilisation}]$$

 Q4. A transistor acts as an amplifier by raising the strength of a weak signal. The d.c. bias voltage applied to the emitter base junction makes it remain in forward bias condition. This forward bias is maintained regardless of the polarity of signal.



Input Resistance

$$R_i = \frac{\Delta V_{BE}}{\Delta I_B}$$

Output Resistance

$$R_o = \frac{\Delta V_{CE}}{\Delta I_C}$$

Current Gain

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

Voltage Gain

$$A_v = \frac{\Delta V_{CE}}{\Delta V_{BE}} = \frac{\Delta I_C \times R_{L \parallel R_o}}{\Delta I_B \times R_i} = \beta \times \frac{R_L}{R_i}$$

R_L = Load Resistance.