

SVKM's NMIMS
MUKESH PATEL SCHOOL OF TECHNOLOGY MANAGEMENT & ENGINEERING/
SCHOOL OF TECHNOLOGY MANAGEMENT & ENGINEERING

Programme: MBA Tech (All Streams)

Year: I

Semester: I

Academic Year: 2018-2019

Subject: Basic Electrical Engineering


Date: 21 November 2018

Marks: 70

Time: 10.00 am to 1.00 pm

Durations: 3 (hrs)

No. of Pages: 04

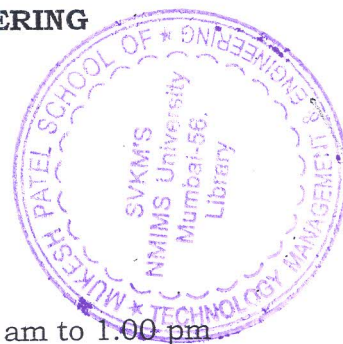


Re Exam (2017-18)

Instructions: Candidates should read carefully the instructions printed on the question paper and on the cover of the Answer Book, which is provided for their use.

- 1) Question No. 01 is compulsory.
- 2) Out of remaining questions, attempt any 04 questions.
- 3) In all 05 questions to be attempted.
- 4) All questions carry equal marks.
- 5) Answer to each new question to be started on a fresh page.
- 6) Figures in brackets on the right hand side indicate full marks.
- 7) Assume suitable data if necessary.

Q. 1)

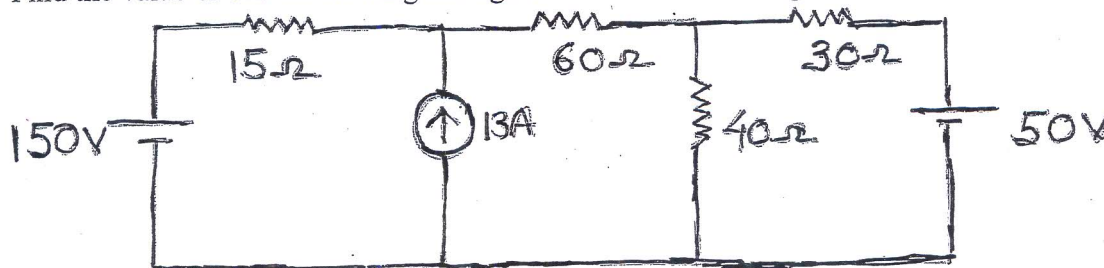- a. Find the value of current flowing through the $30\ \Omega$ resistor using Thevenin's theorem. [05]



- b. Find the average value and rms value of the waveform shown. [03]




- c. Three coils, each having a resistance of $8\ \Omega$ and an inductor of 0.02H are connected in delta to a three-phase 400V , 50Hz . Calculate line current and power absorbed. [03]
- d. Derive the emf equation for a single phase transformer. [03]

Q. 2)

- a. Explain measurement of three phase power using Two Wattmeter method. [06]
- b. Two coils A and B are connected in series across a 240V, 50Hz supply. The resistance of A is $5\ \Omega$ and inductance of B is 0.015 H. If the input from supply is 3KW and 2KVAR Find inductance of coil A and resistance of coil B. Calculate the voltage across each coil. [08]

Q. 3)

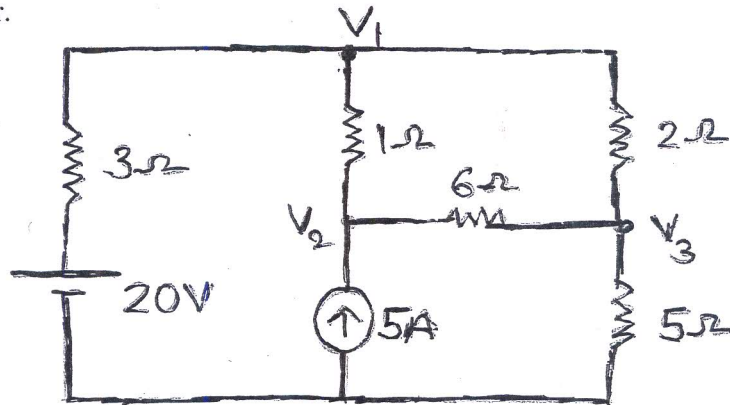- a. Using Nodal analysis, Calculate the node voltages V_1 , V_2 , V_3 and power dissipated in the $6\ \Omega$ resistor. [06]




- b. A 5KVA, 200/400V, 50Hz, single phase transformer gives the following results. [08]

OC test (LV Side)	200V	0.7A	60W
SC test (HV Side)	22V	16A	120W

- (i) Draw the equivalent circuit of the transformer and insert all parameter values.
- (ii) Find efficiency and regulation at 0.9pf (lead) if operating at rated load.
- (iii) Find current at which efficiency is maximum.

Q. 4)

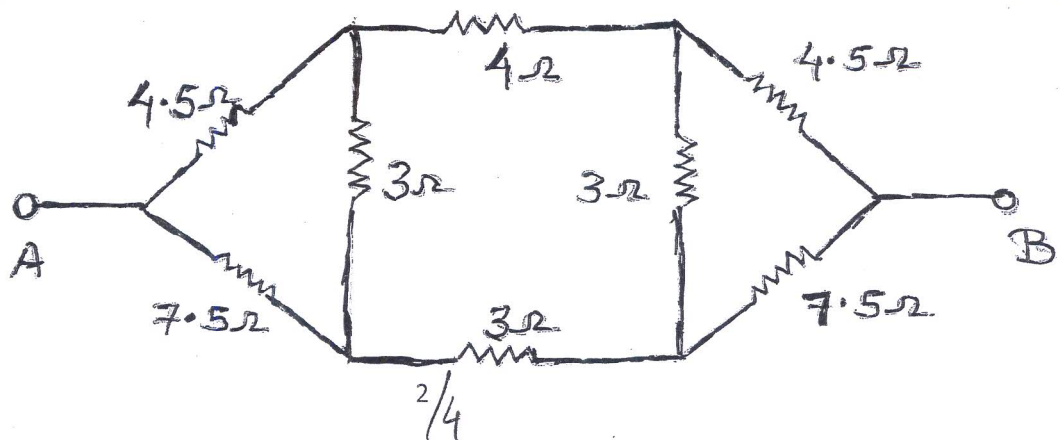- a. Find an equivalent resistance between terminals A and B. [05]



- b. An inductor having a resistance of $25\ \Omega$ and Q_0 of 10 at a resonant frequency of 10KHz is fed from a 100V supply. [05]
Calculate:
(i) Value of series capacitance required to produce resonance with the coil.
(ii) The inductance of the coil.
(iii) Q_0 using L/C ratio.
(iv) Voltage across capacitor
(v) Voltage across coil.
- c. Give the comparison between series and parallel resonance circuit. [04]

Q. 5)


- a. Explain construction and working principle of single phase induction motor. [06]
b. What are the assumption of an ideal transformer? [04]
c. A series R-L-C Circuit of $R=1000\ \Omega$, $L=100\text{ mH}$ and $C=10\mu\text{F}$. The applied voltage across the circuit is 100 V . [04]
(i) Find the resonance frequency of the circuit.
(ii) Find Q of the circuit at resonant frequency.
(iii) Calculate the bandwidth of the circuit.

Q. 6)

- a. A 415V , 50Hz , three-phase voltage is applied to three star-connected identical impedances. Each impedance consists of a resistance of $15\ \Omega$, a capacitance of $177\ \mu\text{F}$ and an inductance of 0.1 henry in series. Find the [08]
(i) Power Factor
(ii) Phase current.
(iii) Line current.
(iv) Active power
(v) Reactive power and
(vi) Total VA.
Draw a neat phasor diagram .If the same impedances are connected in delta, find the line current and power consumed.
- b. Draw the phasor diagram of a single-phase transformer on resistive load and inductive load. [06]

Q. 7)

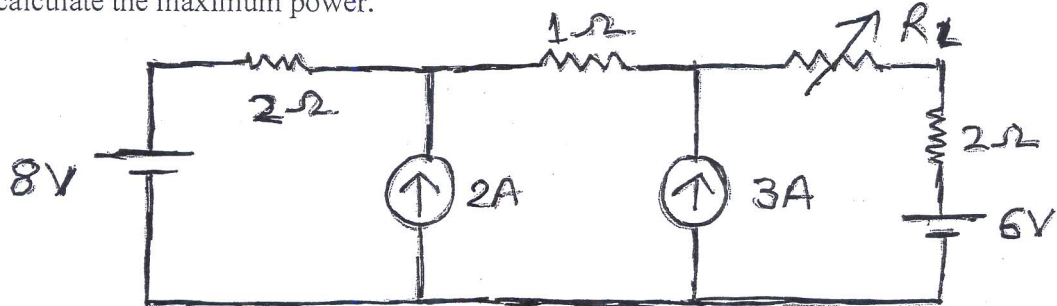- a. For the circuit shown, find the value of the resistance R_L for maximum power transfer and calculate the maximum power. [06]



- b. A three-phase, 10KVA load has a power ^{factor} of 0.342. The power is measured by the Two Wattmeter method. Find the reading of each wattmeter when the
 (i) Power factor is leading.
 (ii) Power factor is lagging. [04]
- c. Explain the types of armature windings used in DC motors. [04]