

SVKM'S NMIMS
School of Technology Management & Engineering, Navi-Mumbai Campus
B.Tech. (Sem- I) (CSBS)
Assignment-4
Subject: Principles of Electrical Engineering
Date of Submission: 01/10/2019

Q.1 Determine the current through 8Ω resistance in the network shown in fig. 1 by Thevenin's theorem.

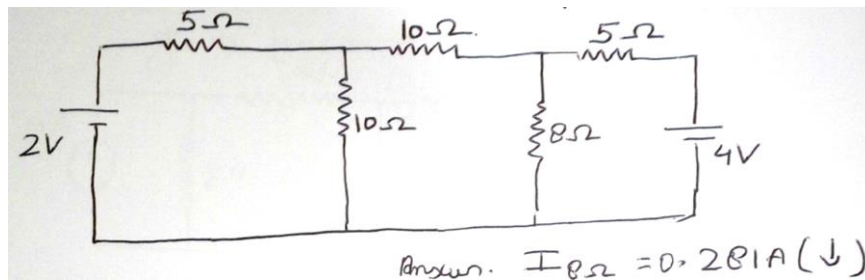


Fig. 1

Q.2 Determine Thevenin equivalent circuit and hence, find the current through 30Ω resistor in network shown in fig. 2.

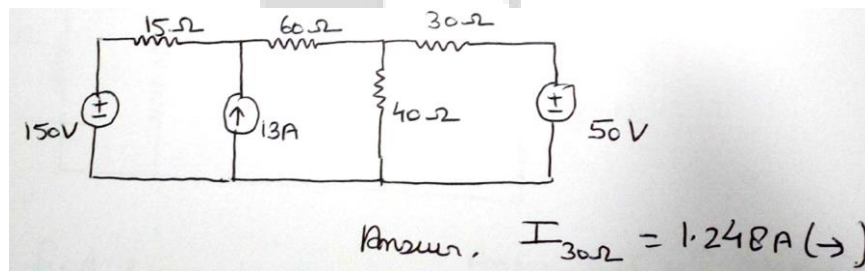


Fig. 2

Q.3 Determine current through 10Ω resistor in network shown in fig. 3 by Thevenin's theorem.

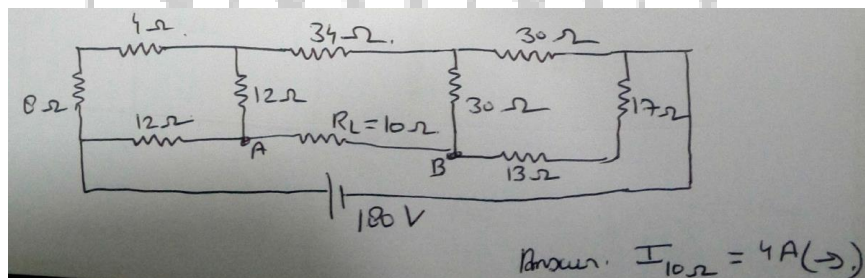


Fig. 3

Q.4 Calculate the current in 5Ω resistor for the network shown in fig. 4.

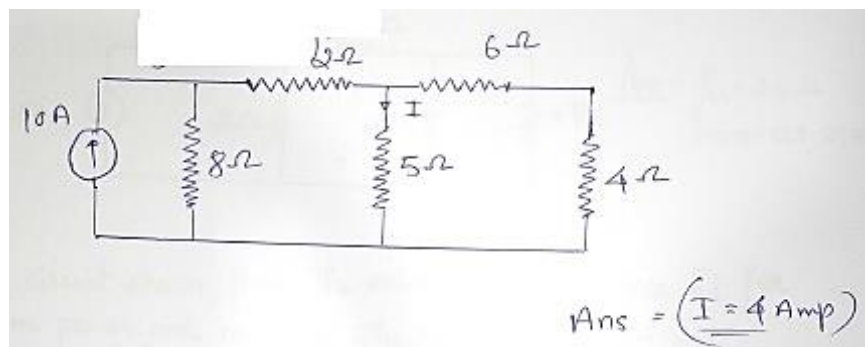


Fig. 4

Q.5 Using Norton's equivalent circuit find current I in the given fig. 5.

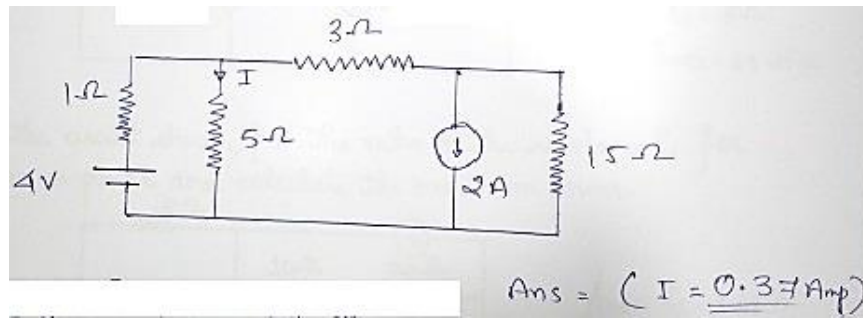


Fig. 5

Q.6 Find current through $R_L = 4\Omega$, and also find power dissipated using Norton's theorem for the circuit of fig. 6.

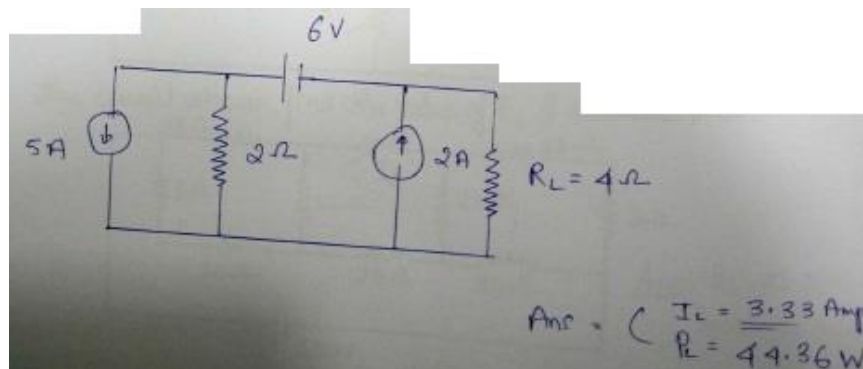


Fig. 6

Q.7 For the circuit shown in fig. 7, find the value of resistance R_L for maximum power transfer and also calculate maximum power.

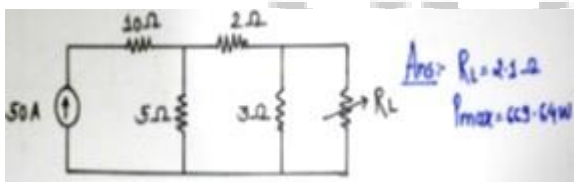


Fig. 7

Q.8 For the circuit shown in fig. 8, find the value of the resistance R_L for maximum power and calculate the maximum power.

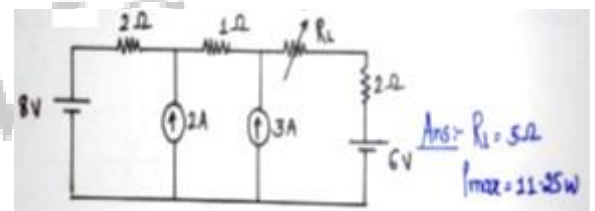


Fig. 8

Q.9 For the circuit shown in fig. 9, find the value of the resistance R_L for maximum power and calculate the maximum power.

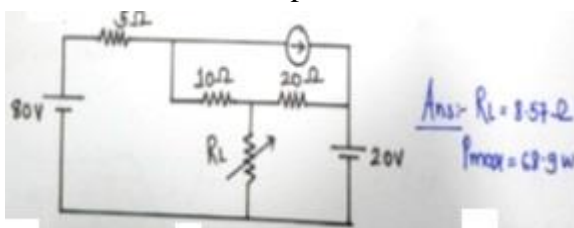


Fig. 9

Q.10 For the circuit shown in fig. 10, find the value of R_L and calculate P_{max} .

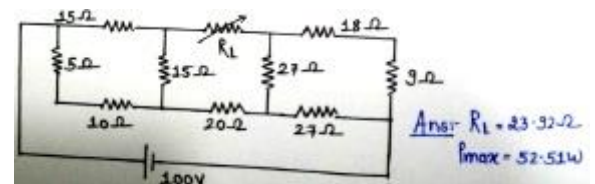


Fig. 10