

# INDEX

## A

Acceptor atoms, **64**  
A.C. equivalent circuit, **248**  
A. C. load line, **251**  
Active region, **475**  
Alpha, **148**  
Amplitude modulation, **414**  
Amplification, **146**  
Amplifier:  
    Class A power, **312**  
    bandwidth, **284**  
    Class B power, **312**  
    Class C power, **313**  
    Class C tuned, **402**  
    direct coupled, **299**  
    distortion in, **311**  
AND gate, **740**  
Anode, **33**  
Antenna, **413**  
Astable multivibrator, **478**  
Audio amplifier, **307**  
Avalanche breakdown, **72**

## B

Band:  
    conduction, **51**  
    valence, **51**  
Bandwidth, **284**

Barrier potential, **67**  
Base, **143**  
Bel power gain, **283**  
Bel voltage gain, **284**  
Beta, **153**  
Binary system, **730**  
Bipolar transistor, **146**  
Bi-stable multivibrator, **482**  
Boolean algebra, **748**  
Breakdown:  
    Avalanche, **72**  
    Zener, **108**  
Bridge rectifier, **92**  
Bypass capacitor, **242**

## C

Capacitor filter, **103**  
Cathode, **33**  
Cathode ray oscilloscope, **616**  
CE amplifier, **164**  
Chassis, **24**  
Chip, semiconductor, **628**  
Choke input filter, **104**  
Clampers, **495**  
Class A operation, **312**  
Class B operation, **312**  
Class C operation, **313**

## 776 ■ Principles of Electronics

Clippers, **487**  
Collector, **143**  
Collector feedback bias, **209**  
Colpitts oscillator, **372**  
CB amplifier, **148**  
Complementary-symmetry, **330**  
Conduction band, **51**  
Constant current source, **9**  
Constant voltage source, **8**  
Coupling capacitor, **242**  
Covalent bond, **56**  
Crystal oscillator, **383**  
Current feedback, **347**  
Current gain, **173**  
Cut-off frequency, **285**

### D

D. C. amplifier, **299**  
D. C. equivalent circuit, **247**  
Decibel, **283**  
Depletion layer, **67**  
Diac, **586**  
Differential amplifier, **664-687**  
Diffusion, **67**  
Digital circuit, **730**  
Diode circuits, **76-124**  
Direct coupling, **299**  
Discrete circuit, **627**  
Distortion, **311**  
Donor atom, **63**  
Doping, **62**  
Double based diode, **590**  
Drain-source curve, **511**  
Driver stage, **325**  
Dynamic resistance, **79**  
Dual-in-line pack, **635**

### E

Efficiency:  
    Half-wave rectifier, **88**

    Full-wave rectifier, **94**  
Electromagnetic deflection, **618**  
Electrons, **4**  
Electron emission, **28-37**  
Electron gun, **617**  
Electron-hole pair, **61**  
Emitter, **143**  
Emitter follower, **349**  
Encoder, **746**  
Energy band theory, **50**  
Equivalent circuit of amplifier, **272**  
Equivalent circuit with signal source, **272**  
Epitaxial layer, **630**  
Exclusive OR gate, **744**  
Extrinsic semiconductor, **62**  
Expression for collector :  
    efficiency, **313**

### F

Feedback, **335**  
Feedback amplifier, **337**  
JFET importance, **510**  
Field effect transistor, **507**  
Field emission, **34**  
Filter circuit, **103**  
Forward bias, **68**  
Forbidden gap, **51**  
Free electron, **6**  
Free-running multivibrator, **478**  
Frequency modulation, **426**  
Frequency response, **283**

### G

Gain:  
    power, **173**  
    voltage, **173**  
    gate, **507**  
    ground, **24**

### H

Hartley oscillator, **374**

Holding current, 558  
 Hole current, 61  
 Heat sink, 322  
 Hybrid, 643

**I**

Inductor filter, 104  
 Insulated gate, 536  
 Integrated circuit, 628  
 Interstage coupling, 281  
 Intermediate frequency, 434  
 Intrinsic semiconductor, 62  
 Intrinsic stand off ratio, 592  
 Impedance matching, 296  
 Input impedance, 172

**J**

Junction, pn, 66  
 Junction diode, 77  
 Junction transistor, 142

**K**

Knee voltage, 72

**L**

Large signal operation, 312  
 LC oscillators, 371-376  
 Leakage current, 71  
 Light-emitting diode (LED), 126  
 Load D.C. and A.C., 248, 249  
 Load line:  
     a.c., 251  
     d.c., 249  
 Local oscillator, 433  
 Logic gates, 738

**M**

Max. A.C. power output, 314  
 Max. collector efficiency, 314  
 Majority carriers, 65  
 Microelectronics, 627  
 Minority carriers, 65  
 Modulation:

    AM, 414  
     FM, 426  
 Monolithic IC, 629  
 MOSFET, 535  
 Multicolour LEDs, 128  
 Multivibrators :  
     astable, 478  
     bistable, 482  
     monostable, 480

**N**

NAND gate, 742  
 Negative feedback, 336  
 n-p-n transistor, 142  
 n-type semiconductor, 62  
 Noise, 311  
 NOR gate, 743  
 NOT gate, 742

**O**

Operational Amplifiers, 662-728  
     Block diagram, 663  
     Input/output Polarity relation, 689  
     Voltage gain, 688  
     Values of supply voltage, 690  
 Optoisolator, 133  
 OR gate, 739  
 Oscillators:  
     Collpits, 372  
     Crystal, 383  
     Hartley, 374  
     L.C., 371-376  
     Phase shift, 377  
     Tuned collector, 371  
     Wein bridge, 378  
 Oscilloscope, 616  
 Output resistance, 172  
 Over voltage detector, 595  
 Oxide coated emitter, 32

**P**

p-type semiconductor, 64  
 Peak inverse voltage, 73  
 Pentavalent atoms, 63

## 778 ■ Principles of Electronics

Phase-shift oscillator, 377  
Photo-diode, 130  
Photo-emission, 35  
Piezo-electric effect, 380  
 $\pi$ -filter, 104  
Pinch off voltage, 513  
 $p$ - $n$ -junction, 66  
 $p$ - $n$ - $p$  transistor, 142  
Positive clipper, 487  
Power dissipation, 311  
Power gain, 173  
Push-pull amplifier, 326

### Q

Quartz crystal, 381  
Quiescent point, 167

### R

RC differentiator, 483  
RC integrator, 486  
RC oscillator, 377  
RC coupling, 289  
Rectifiers, 87  
Relaxation oscillator, 595  
Reverse bias, 68  
Ripple factor, 101

### S

Saturation collector current, 473  
Saturation region, 474  
Sawtooth wave, 619  
Secondary emission, 34  
SCR, 555  
Semiconductors, 56  
Shockley diode, 137  
Sideband frequencies, 418  
Stabilisation, 197  
Stand off voltage, 592  
Substrate, 629  
Superhetrodyne receiver, 433

### T

Thermal runaway, 197  
Thermionic emission, 30  
Thevenin's theorem, 15  
Thyristor, 555  
Transformer coupling, 294  
Transistor:  
    AM modulator, 419  
    CB, 148  
    CC, 162  
    CE, 152

Trivalent impurity, 64  
Tuned collector oscillator, 371  
Tunnel diode, 134

### U

Uni-junction transistor, 589  
Unipolar transistor, 510

### V

Varactor-diode, 136  
Voltage divider bias, 212  
Voltage regulator, 448  
Voltmeter, electronic, 609

### W

Wein bridge oscillator, 378  
Window, 631

### X

X-cut, 380

### Y

Y-cut, 380

### Z

Zener breakdown, 108  
Zener diode, 108  
Zener diode regulator, 110  
Zener symbol, 109