

SVKM'S NMIMS
School of Technology Management & Engineering, Navi-Mumbai Campus
B.Tech. (Sem- I) (CSBS)
Assignment-1
Subject: Principles of Electrical Engineering
Date of Submission: 27/08/2019

- Q.1 Calculate the effective resistance R_{AB} of a network shown in fig.1.

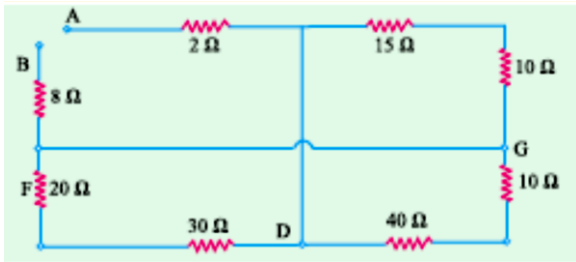


Fig. 1

- Q.2 Find the current through lamp when switch s is closed in the circuit shown in fig. 2.

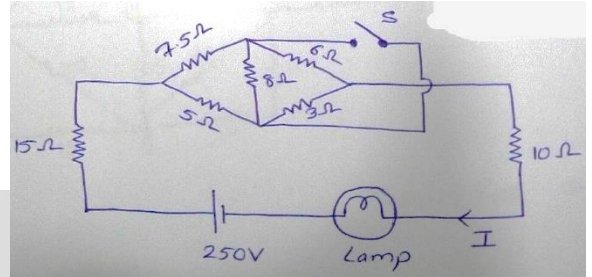


Fig. 2

- Q.3 Calculate the effective resistance of the circuit of fig. 3 and the current through 8Ω resistance, when potential difference of 60 V is applied between the points A and B.

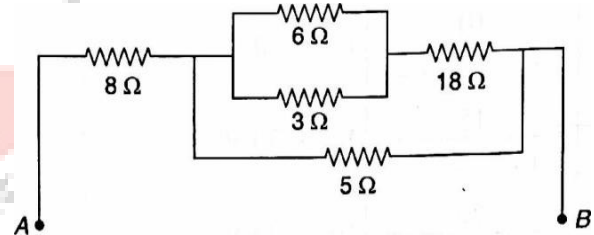


Fig. 3

- Q.4 What is reading of the ammeter shown in the circuit shown in fig. 4?

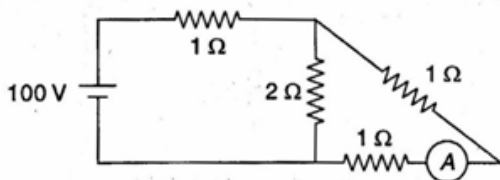


Fig. 4

- Q.5 Calculate the effective resistance R_{AB} of network of fig.5.

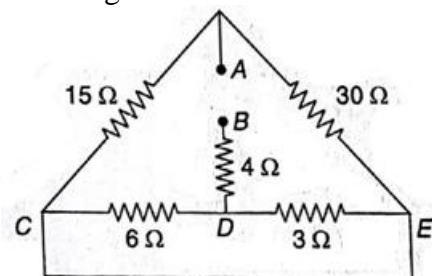


Fig. 5

- Q.6 Calculate the equivalent resistance between terminal A & B of circuit shown in fig. 6.

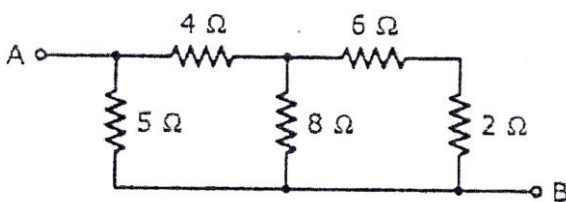


Fig. 6

- Q.7 For the circuit shown in fig. 7, find the value of resistance R , when power consumed by 12Ω resistance is 36W .

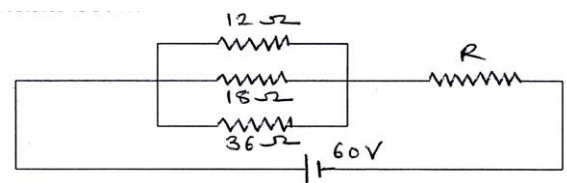


Fig. 7

Q.8 Find the equivalent resistance of the network of Fig. 8 between terminals A and B . All resistance values are in ohms.

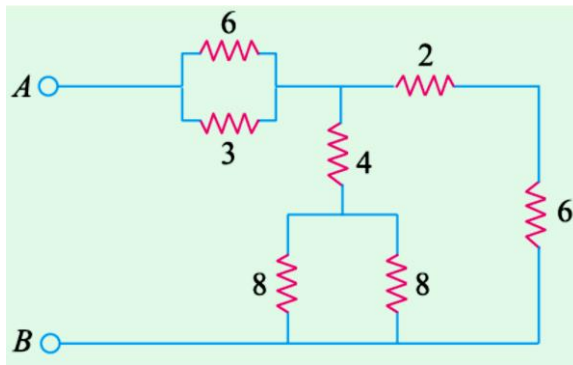


Fig. 8

Q.9 Compute the value of battery current I in Fig. 9. All resistances are in ohm.

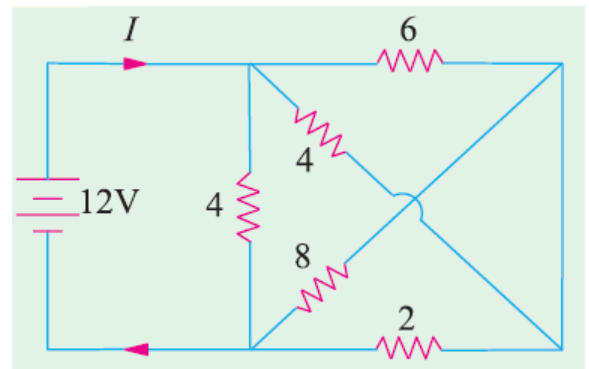


Fig. 9

Q.10 Compute the equivalent resistance of the circuit of Fig. 10 (a) between points (i) ab (ii) ac and (iii) bc . All resistances values are in ohm.

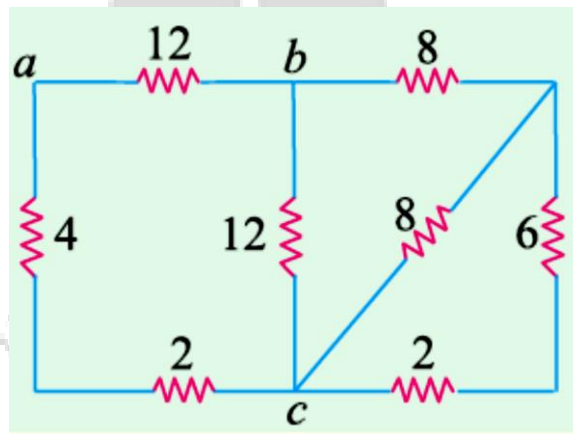


Fig. 10